

# CONTENTS IN DETAIL

Foreword by Joe Grand . . . . .	xix
Acknowledgments . . . . .	xxi

## **INTRODUCTION** **XXIII**

About This Book . . . . .	xxiv
Who Should Read This Book . . . . .	xxiv
How to Read This Book. . . . .	xxiv
What's in This Book?. . . . .	xxv
Your Electronics Lab . . . . .	xxvii
Useful Supplies . . . . .	xxviii
Safety First! . . . . .	xxviii

## **PART 1: PLAYING WITH ELECTRICITY**

### **1** **WHAT IS ELECTRICITY?** **3**

Project #1: Turn on a Light! . . . . .	4
Shopping List . . . . .	4
Step 1: Inspect the Light Bulb . . . . .	4
Step 2: Connect the Light Bulb to the Battery . . . . .	5
How Does Electricity Light a Bulb? . . . . .	5
What Is an Electron? . . . . .	6
Voltage Pushes Electrons . . . . .	6
Current Flows . . . . .	7
Resistance Reduces Current. . . . .	7
Lighting the Bulb . . . . .	8
How Is a Circuit Like a Pipe System? . . . . .	9
Meet the Switch . . . . .	10
Project #2: Intruder Alarm . . . . .	11
Shopping List . . . . .	12
Tools . . . . .	13
Step 1: Does the Buzzer Beep? . . . . .	13
Step 2: Prepare the Aluminum. . . . .	14
Step 3: Foil Your Door. . . . .	15
Step 4: Prepare a Trigger Wire . . . . .	15
Step 5: Connect the Buzzer and Trigger Wire. . . . .	16
Step 6: Mount the Buzzer and Trigger Wire . . . . .	16
Step 7: Add a Power Source . . . . .	17

Step 8: Stage an Intruder Alert! . . . . .	17
Step 9: What If the Intruder Alarm Doesn't Work? . . . . .	17
What's Next? . . . . .	18

## **2** **MAKING THINGS MOVE WITH ELECTRICITY AND MAGNETS**

**19**

How Magnets Work . . . . .	20
<i>Try It Out: Find Some Magnetic Objects!</i> . . . . .	21
Meet the Electromagnet . . . . .	22
Project #3: Create Your Own Electromagnet . . . . .	23
Shopping List . . . . .	24
Tools . . . . .	25
Step 1: Check Your Bolt . . . . .	25
Step 2: Remove Insulation from One End of the Coil Wire . . . . .	26
Step 3: Wind the Wire . . . . .	27
Step 4: Connect the Negative Battery Terminal to the Coil . . . . .	28
Step 5: Connect the Switch . . . . .	28
Step 6: Test Your Super Electromagnet . . . . .	30
Step 7: What If the Electromagnet Isn't Working? . . . . .	31
Meet the Motor . . . . .	31
Project #4: Create a Motor . . . . .	32
Shopping List . . . . .	34
Tools . . . . .	35
Step 1: Create the Rotor . . . . .	35
Step 2: Build the Motor's Structure . . . . .	36
Step 3: Place the Magnets . . . . .	37
Step 4: Reinsulate Part of the Coil . . . . .	38
Step 5: Rev Up Your Motor . . . . .	39
Step 6: What If the Motor Doesn't Work? . . . . .	40
What's Next? . . . . .	41

## **3** **HOW TO GENERATE ELECTRICITY**

**43**

Generating Electricity with Magnets . . . . .	44
A Changing Magnetic Field Creates Electricity . . . . .	44
How Does a Generator Work? . . . . .	45
<i>Creating Electricity from Water or Wind</i> . . . . .	46
Meet the Multimeter . . . . .	47
How to Measure Voltage . . . . .	47
What Are AC and DC? . . . . .	48

Project #5: Make a Shake Generator . . . . .	49
Shopping List . . . . .	50
Tools . . . . .	50
Step 1: Prepare Your Tube . . . . .	51
Step 2: Wind Your Coil . . . . .	52
Step 3: Connect the Multimeter . . . . .	52
Step 4: Shake That Thing! . . . . .	53
Step 5: What If There's No Voltage? . . . . .	54
<i>Try It Out: Using a Motor as a Generator</i> . . . . .	55
How Do Batteries Work? . . . . .	55
What's Inside a Battery? . . . . .	55
The Chemistry Behind Batteries . . . . .	56
What Determines a Battery's Voltage? . . . . .	57
Project #6: Turn On a Light with Lemon Power . . . . .	58
Meet the LED . . . . .	58
Shopping List . . . . .	59
Tools . . . . .	60
Step 1: Prepare Your Wires . . . . .	60
Step 2: Insert Electrodes into a Lemon . . . . .	61
Step 3: Create Four Lemon Batteries . . . . .	62
Step 4: Connect the Lemons in Series . . . . .	62
Step 5: Test Your Lemon Battery . . . . .	64
<i>Try It Out: More Food Batteries!</i> . . . . .	65
Step 6: What If Your Lemon Light Doesn't Work? . . . . .	65
What's Next? . . . . .	66

## PART 2: BUILDING CIRCUITS

<b>4</b>		
<b>CREATING LIGHT WITH LEDs</b>		<b>69</b>
Meet the Resistor . . . . .		70
Resistor Color Codes . . . . .		70
<i>How to Write Large Values</i> . . . . .		72
What Are Resistors Made Of? . . . . .		72
Resistors Control Current and Voltage . . . . .		73
Introducing Ohm's Law . . . . .		73
Project #7: Let's Destroy an LED! . . . . .		74
Shopping List . . . . .		75
Step 1: Identify Which LED Leg Is Which . . . . .		75
Step 2: Break That LED! . . . . .		76
Step 3: What If Nothing Happens to the LED? . . . . .		76

How to Use an LED Correctly . . . . .	76
<i>How to Write Small Values</i> . . . . .	77
Protecting Your LED with a Resistor . . . . .	77
Calculating the Resistance You Need . . . . .	78
Project #8: Powering an LED . . . . .	78
Shopping List . . . . .	79
Step 1: Twist the Resistor and LED. . . . .	79
Step 2: Wire the Battery Clip. . . . .	80
Step 3: Let There Be Light! . . . . .	80
Step 4: What If the LED Doesn't Work? . . . . .	81
Building Circuits on a Breadboard . . . . .	81
How to Connect Components and Wires . . . . .	81
Wires to Use on a Breadboard . . . . .	83
Project #9: Your First Breadboard Circuit . . . . .	84
Shopping List . . . . .	84
Step 1: Place the Resistor . . . . .	85
Step 2: Place the LED . . . . .	85
Step 3: Place the Battery Clip . . . . .	86
Step 4: What If the LED Doesn't Work? . . . . .	87
What's Next? . . . . .	87

## **5**

### **BLINKING A LIGHT FOR THE FIRST TIME** **89**

Meet the Capacitor . . . . .	90
How Capacitors Work . . . . .	90
Polarized and Nonpolarized Capacitors. . . . .	91
Capacitor Values . . . . .	92
Project #10: Test a Capacitor . . . . .	92
Shopping List . . . . .	93
Step 1: Start with the LED Circuit . . . . .	94
Step 2: Add the Capacitor. . . . .	94
Step 3: Charge the Capacitor . . . . .	95
Step 4: Use the Capacitor to Light the LED . . . . .	95
Step 5: What If the Circuit Doesn't Work? . . . . .	95
Describing Circuits with Symbols . . . . .	95
Meet the Relay . . . . .	97
Using the Relay to Blink a Light . . . . .	99
Slowing Down the Blinking . . . . .	100
Project #11: Blink a Light! . . . . .	101
Shopping List . . . . .	102
Step 1: Identify the Relay Pins. . . . .	103
Step 2: Make the Relay Switch Fast . . . . .	104

Step 3: Make the Relay Stay On Longer . . . . .	105
Step 4: Make the Relay Stay Off Longer . . . . .	106
Step 5: Add the LED and Resistor . . . . .	106
Step 6: What If the LED Won't Blink? . . . . .	108
<i>Try It Out: Make Your Intruder Alarm More Effective.</i> . . . . .	108
What's Next? . . . . .	109

## **6 LET'S SOLDER! 111**

How to Solder . . . . .	112
Soldering Safety Tips . . . . .	113
Heat the Soldering Iron . . . . .	114
Clean the Soldering Iron Tip . . . . .	115
Tin the Soldering Iron Tip . . . . .	115
Heat Both the Pin and the Pad . . . . .	115
Add Solder . . . . .	116
Remove the Soldering Iron . . . . .	116
Watch Out for Bad Solder Joints! . . . . .	117
Project #12: Solder Your First LED Circuit . . . . .	118
Shopping List . . . . .	118
Tools . . . . .	119
Step 1: Place the Components . . . . .	120
Step 2: Bend the Component Legs . . . . .	120
<i>How to Read the Circuit Board Illustrations</i> . . . . .	121
Step 3: Heat and Clean the Soldering Iron . . . . .	122
Step 4: Solder the Resistor and LED . . . . .	122
Step 5: Trim the Legs . . . . .	122
Step 6: Solder the Battery Clip . . . . .	123
Step 7: Let There Be Light! . . . . .	124
Step 8: What If the Soldered LED Circuit Doesn't Work? . . . . .	124
Oops! How Do I Remove a Soldered Component? . . . . .	125
Project #13: Desolder the Battery Clip . . . . .	126
Shopping List . . . . .	126
Tools . . . . .	126
Step 1: Heat the Soldering Iron . . . . .	127
Step 2: Place the Solder Wick on the Solder Joint . . . . .	127
Step 3: Heat the Solder Joint and the Solder Wick . . . . .	128
Step 4: Trim the Used Solder Wick . . . . .	128
Step 5: Remove the Other Battery Clip Wire . . . . .	129
<i>Try It Out: Solder More Stuff!</i> . . . . .	129
What's Next? . . . . .	130

**7**  
**CONTROLLING THINGS WITH ELECTRICITY** **131**

Meet the Transistor . . . . . 132  
    Why Use a Transistor? . . . . . 133  
    How the Transistor Works . . . . . 134  
    Controlling an LED with a Transistor. . . . . 135  
Project #14: Build a Circuit that Senses Touch . . . . . 136  
    Shopping List . . . . . 138  
    Tools . . . . . 139  
    Step 1: Place Components on the Prototyping Board . . . . . 140  
    Step 2: Check Your Component Placement . . . . . 140  
    Step 3: Solder the Components and Trim Excess Legs. . . . . 140  
    Step 4: Solder the Touch Pad . . . . . 141  
    Step 5: Power It Up! . . . . . 142  
    Step 6: Test the Sensor . . . . . 142  
    Step 7: What If the Touch Sensor Doesn't Work? . . . . . 142  
    *Try It Out: Can the Touch Sensor Detect Different Touches?* . . . . . 144  
Resistors That Can Change Value. . . . . 144  
    Meet the Potentiometer . . . . . 145  
    Meet the Photoresistor . . . . . 146  
Dividing a Voltage with Resistors . . . . . 146  
    What Does a Voltage Divider Look Like? . . . . . 147  
    Calculating the Voltage from a Voltage Divider . . . . . 147  
    How a Voltage Divider Can Help Measure Light . . . . . 148  
Project #15: Build a Sunrise Wake-Up Alarm. . . . . 148  
    Shopping List . . . . . 150  
    Tools . . . . . 151  
    Step 1: Place Components on the Prototyping Board . . . . . 152  
    Step 2: Solder the Components and Trim the Legs. . . . . 152  
    Step 3: Add the Buzzer to the Board . . . . . 153  
    Step 4: Make the Remaining Connections with Wires . . . . . 154  
    Step 5: Add the Battery Clip to the Board. . . . . 155  
    Step 6: Set a Wake-Up Call . . . . . 156  
    Step 7: What If There's No Sound? . . . . . 156  
    *Try It Out: Temperature-Controlled Fan* . . . . . 157  
What's Next? . . . . . 159

**8**  
**BUILDING A MUSICAL INSTRUMENT** **161**

Meet the Integrated Circuit . . . . . 162  
ICs and Datasheets. . . . . 162  
How to Make Sound with Electricity. . . . . 163

Sounds That Humans Can Hear . . . . .	164
Meet the 555 Timer. . . . .	164
Powering an IC . . . . .	165
How to Set the Output Speed of the 555 Timer . . . . .	166
Project #16: Make Your Own Sound with the 555 Timer. . . . .	167
Shopping List . . . . .	169
Step 1: Place the 555 Timer on the Breadboard . . . . .	170
Step 2: Set the Frequency. . . . .	171
Step 3: Connect the Speaker and Coupling Capacitor . . . . .	171
Step 4: Connect the Power and Reset Pins . . . . .	173
Step 5: Make Some Sound! . . . . .	173
Step 6: What If There’s No Sound? . . . . .	174
<i>Checking Connections as a Team</i> . . . . .	174
Turning an Annoying Beep into Music . . . . .	175
Project #17: An Instrument That Beeps and Boops . . . . .	175
Shopping List . . . . .	177
Step 1: Connect the 555 Timer and the Capacitors. . . . .	178
Step 2: Connect Jumper Wires. . . . .	179
Step 3: Connect the Note Controller and Resistor . . . . .	179
Step 4: Add the “On” Button. . . . .	180
Step 5: Add the Loudspeaker . . . . .	181
Step 6: Play Some Music! . . . . .	182
Step 7: What If the Instrument Doesn’t Work? . . . . .	183
<i>Try It Out: Make a Motion-Controlled Instrument.</i> . . . . .	183
What’s Next? . . . . .	184

## PART 3: THE DIGITAL WORLD

<b>9</b>	
<b>HOW CIRCUITS UNDERSTAND ONES AND ZEROS</b>	<b>187</b>
Ones and Zeros as Voltages . . . . .	188
Meet the Binary Number System . . . . .	188
Project #18: Convert from Binary to Decimal . . . . .	190
Tools. . . . .	190
Step 1: Write It Down on Paper . . . . .	190
Step 2: Write the Position Values . . . . .	191
Step 3: Find the Value of Each Digit . . . . .	191
Step 4: Add the Numbers . . . . .	192
<i>Try It Out: Transform More Binary Numbers</i> . . . . .	192
Bits and Bytes. . . . .	193
Numbers Can Be Anything . . . . .	193

Project #19: Color Guessing Game . . . . .	194
Meet the RGB LED . . . . .	195
Shopping List . . . . .	196
Step 1: Place the Color Chooser’s Push Buttons . . . . .	197
Step 2: Connect the RGB LED . . . . .	198
Step 3: Connect the Color Revealer Button . . . . .	198
Step 4: Test the Colors . . . . .	199
Step 5: What If the Game Doesn’t Work? . . . . .	200
<i>Try It Out: Solder the Color Guessing Game</i> . . . . .	200
How Binary Numbers Can Create Words . . . . .	201
Project #20: The Secret Message Machine . . . . .	202
Meet the DIP Switch . . . . .	204
Shopping List . . . . .	204
Step 1: Connect the Push Button . . . . .	205
Step 2: Connect the DIP Switch . . . . .	206
Step 3: Connect the LEDs . . . . .	207
Step 4: Send a Secret Message! . . . . .	209
Step 5: What If the Secret Message Machine Doesn’t Work? . . . . .	211
<i>Why Computers Use Ones and Zeros</i> . . . . .	211
What’s Next? . . . . .	212

## 10 **CIRCUITS THAT MAKE CHOICES** **213**

It’s Only Logical . . . . .	214
Meet the Logic Gates . . . . .	215
AND Gates Check for Two True Inputs . . . . .	216
OR Gates Check for One True Input . . . . .	216
NOT Gates Flip Inputs . . . . .	217
A Bigger AND Gate . . . . .	217
How to Draw Logic Circuit Diagrams . . . . .	218
A Logic Equation for a Secret Code . . . . .	218
Converting a Logic Equation into a Circuit Diagram . . . . .	219
<i>Try It Out: Draw More Logical Statements as Circuits</i> . . . . .	220
Using Logic Gates in Real Life . . . . .	220
<i>More About Current, Components, and Transistors</i> . . . . .	222
Project #21: A Secret Code Checker . . . . .	223
Shopping List . . . . .	224
Tools . . . . .	225
How to Use Other Voltages with a Breadboard . . . . .	226
<i>Making Circuits More Reliable</i> . . . . .	227
Step 1: Place the Switches and Resistors . . . . .	228
Step 2: Place the ICs . . . . .	228
Step 3: Place the Transistor and LED . . . . .	229



Step 4: Build the Logic Circuit . . . . .	230
Step 5: Finish Wiring the Transistor . . . . .	233
<i>Protecting Your Components</i> . . . . .	234
Step 6: Power and Test the Secret Code Checker . . . . .	234
Step 7: What If the LED Doesn't Light Up? . . . . .	235
<i>Try It Out: Disarm Your Intruder Alarm</i> . . . . .	236
Negative Logic Gates . . . . .	237
NAND Looks for One False Input . . . . .	237
NOR Looks for Two False Inputs . . . . .	237
What's Next? . . . . .	238

## **11** **CIRCUITS THAT REMEMBER INFORMATION** **239**

Saving One Bit at a Time . . . . .	240
A Better Memory Circuit . . . . .	241
Memory That Changes Only at a Certain Time . . . . .	241
An Output That Toggles . . . . .	244
Project #22: An Electronic Coin Tosser . . . . .	245
Shopping List . . . . .	247
Step 1: Build the Oscillator Circuit . . . . .	248
Step 2: Add the Start Button . . . . .	249
Step 3: Build the Toggle Circuit . . . . .	251
Step 4: Add the Heads and Tails LEDs . . . . .	252
Step 5: Toss that "Coin"! . . . . .	253
Step 6: What If the Coin Tosser Doesn't Work? . . . . .	254
What's Next? . . . . .	255

## **12** **LET'S MAKE A GAME!** **257**

Meet the Reaction Game Circuits . . . . .	259
Meet the $V_{CC}$ and GND Symbols . . . . .	259
<i>Why Is It Called <math>V_{CC}</math>?</i> . . . . .	260
A 555 Timer to Set the Light Speed . . . . .	260
A Counter to Turn the LEDs On . . . . .	262
A Latch to Start and Stop the Light . . . . .	263
Project #23: An LED Reaction Game . . . . .	265
Shopping List . . . . .	267
Tools . . . . .	268
Step 1: Build the 555 Timer Circuit . . . . .	269
Step 2: Build the LED-Controlling Circuit . . . . .	270
Step 3: Build the Start and Stop Circuit . . . . .	274
Step 4: Practice Your Reaction Time! . . . . .	276

Step 5: What If the Game Isn't Working? .....	276
<i>Try It Out: Change the Light's Speed</i> .....	278
Add a Buzzer to Your Game .....	279
What's Next? Go Make Cool Stuff! .....	280

## **HANDY RESOURCES** **281**

Component and Unit Value Cheat Sheets. ....	282
Resistor Color Codes .....	282
Capacitor Codes. ....	283
Standard Prefixes .....	284
A Quick Review of Ohm's Law .....	284
A Basic Voltage Divider Circuit .....	285
Online Electronics Shops .....	286
Online Resources. ....	286

## **INDEX** **289**

